

中山大学本科生期末考试

考试科目：《数字电路》（A 卷）

学年学期：2017 学年第二学期

姓 名：_____

学 院/系：电子与信息工程学院

学 号：_____

考试方式：闭卷

年级专业：_____

考试时长：120 分钟

班 别：_____


警示

《中山大学授予学士学位工作细则》第八条：“考试作弊者，不授予学士学位。”


-----以下为试题，共 2 道大题，总分 100 分,考生请在答题纸上作答-----

一、填空题（共 25 小题，每个答案 2 分，共 50 分）


- Convert the decimal -86 to signed binary(把十进制数-86 转为带符号二进制数):_____;
- Convert decimal number 0.32 to binary number (six significant bits) (把小数 0.32 转为具有六位有效数字的二进制数):_____;
- The 2's complement of 100101 (100101 的补码) is:_____;
- Convert binary number 10010 to gray code (把二进制数 10010 转为格雷码):_____;
- The odd parity bit for 1100 0011 is (数据 1100 0011 的奇校验位是):_____;
- The detailed expression for $X = A \oplus B$ ($X = A \oplus B$ 的具体表达式) is:_____;
- Convert $X = (\bar{A}+B)(A+B+C)$ to standard POS form (把 $X = (\bar{A}+B)(A+B+C)$ 转化为标准 POS):_____;
- The circuit shown is equivalent to (图所示电路等效为哪种逻辑门):_____;
- The circuit shown will have identical logic out if all gates are changed to (当所示电路中的所有门电路换成何种逻辑门，该电路的逻辑功能保持不变):_____;
- Comparators can be expanded using the configuration as shown (比较器可用如下所示方式进行扩展). The comparator which represents LSB is (表达低位的比较器是):_____;

 

(Question. 8)

 


(Question. 9)

 


(Question. 10)

- The time interval illustrated is called (图中的时间间隔称为):_____;

12. If the output signal of a one shot circuit is obtained as follow, determine whether this one shot is retriggerable or not ? (如果一个单稳电路的输出信号如下图所示，确定这个单稳是否可重复触发?) : ____;

 


(Question. 11)

 


(Question. 12)

13. The given circuit based on 555 timer is a (图中所示基于 555 定时器的电路为): ____;
14. For the given circuit, assume the input frequency (f_{in}) is 512 Hz (对于给定电路，假设输入信号频率 f_{in} 为 512 Hz), the output frequency (f_{out}) will be (则输出信号频率 f_{out} 为): ____;

 


(Question. 13)

 


(Question. 14)

15. The delay time caused by a 8-bit serial-in/ serial-out shift register is (一个八位串入/串出移位寄存器提供的延迟时间为) : ____ clock period(s) (时钟周期);
16. If the present state for a 4-bit Johnson counter is 1100 (如果一个四位 Johnson Counter 的当前状态是 1100), the next state is (那么下一个状态是): ____;
17. The main advantage of static RAM compared to dynamic RAM is (相比于动态 RAM, 静态 RAM 的主要优点为): ____;
18. Among Mask ROM, PROM and EEPROM (在 Mask ROM, PROM 和 EEPROM 中), which cell is erasable? (哪种 ROM 可擦除?) : ____;
19. Which type of memory expansion is implemented using the circuit shown? (图中所示电路是用来实现何种内存扩展?) : ____;
20. The number of comparators required in a 8-bit flash ADC is (一个 8 位快速 ADC 中所需要的比较器数目是): ____;
21. The ADC circuit shown is a (图中所示是哪种类型 ADC 电路): ____;

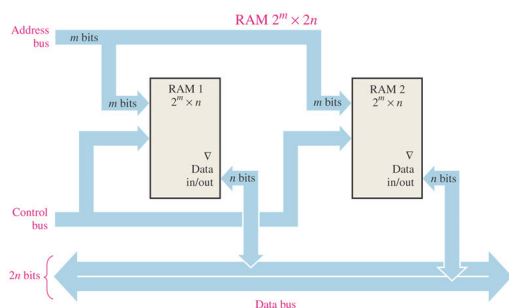


(Question. 19)

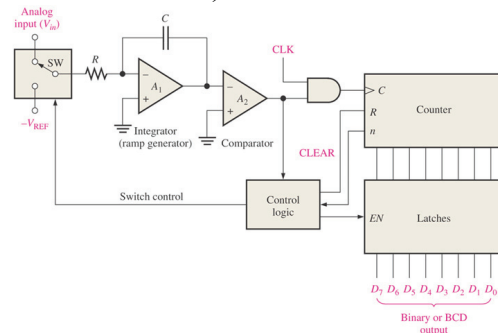


(Question. 21)


22. The DAC circuit shown is a (图中所示是哪一种类型 DAC 电路): ____;
23. What is the logic function performed by the circuit? (该电路实现的逻辑功能是?): ____;
24. Will Q2 be on or off for the given inputs? (给定以下输入 A、B 的组合, Q2 是导通或截止?)
- A=Low, B=Low: ____; A=Low, B=High: ____;

 

(Question. 22)

 


(Question. 23)

 

(Question. 24)


二、分析设计题 (共 4 小题, 共 50 分)

1. Write the output expression for the circuit shown below, obtain the truth table according to the expression, and determine the logic function. (写出所示逻辑电路的输出表达式, 列出真值表, 并确定其逻辑功能) (8 points)

 


(Question. 1)

2. Design a 1 bit full subtractor (设计一个一位全减器来计算 $A-B-C$), which computes $A-B-C$, where C is the borrow from the next less significant digit (其中 C 是来自低位的借位). It produce a difference D and a borrow from the next more significant bit P. (它将得到差 D 和对高位的借位 P)
- (a) Implement the full subtractor by gates (write down the logic functions for the D and P, don't draw the circuit diagram) (采用逻辑门实现这个全减器, 只需写出 D 和 P 的逻辑表达式, 不需要画出电路图) (8 points)
- (b) Implement the full subtractor by 74LS153 multiplexer and some gates (draw the circuit diagram). 74HC153 has two identical 4-input multiplexers which select two bits of data from up to four sources according to common data select inputs. (采用 74LS153 和逻辑门来实现这个全减器, 需画出具体电路图, 其中 74HC153 包含两个四输入多路复用器) (4 points)

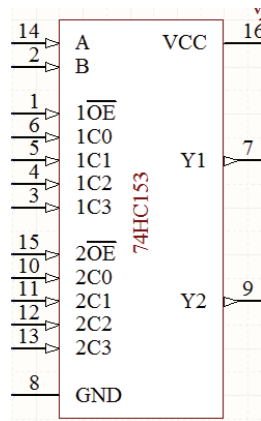

(Question. 2)

3. Determine the logic function of the circuit sketched below. (确定下图所示电路的逻辑功能) The detailed procedure is required. (需给出具体过程) (14 points)

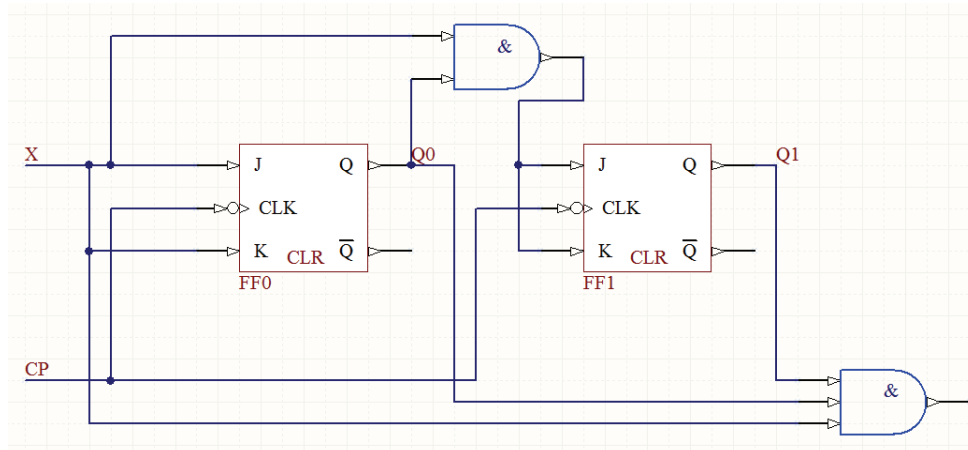

(Question. 3)

4. Design a synchronous modulus-5 counter using D flip-flops and necessary gates(用 D 触发器和必要逻辑门设计一个同步模-5 计数器). The counter is required to go through the following sequence: 0->2->4->1->3->0->.... (要求计数器产生以下时序: 0, 2, 4, 1, 3, 0,...) The detailed procedure is required. (需给出具体过程). (16 points)